

# **CPU Architecture**

**LAB1 preparation report**

**VHDL part1 – Concurrent code**

**Hanan Ribo**

**24/03/2022**

## Table of contents

1. Aim of the Laboratory .....	3
2. System Design ISA.....	3
3. System Design Micro-Architecture .....	4
4. Generic Adder/Subtractor module based on a single ripple carry adder:.....	5
5. Shifter Module based on a single Barrel-Shifter n-bit:.....	6
6. Test and Timing:.....	6
7. System Output Example (for n=8) .....	7
8. Requirements .....	9
9. Grading Policy .....	10

## 1. Aim of the Laboratory

- Obtaining skills in VHDL part1 code, which contains Code Structure, Data Types, Operators and Attributes, Concurrent Code, Design Hierarchy, Packages and Components.
- Obtaining basic skills in ModelSim (multi-language HDL simulation environment).
- General knowledge rehearsal in digital systems.
- Proper analysis and understanding of architecture design.

## 2. System Design ISA

Function Kind	Decimal value	ALUFN	Operation	Note
Arithmetic	8	01000	Res=Y+X	
	9	01001	Res=Y-X	Used also for compare operation
	10	01010	Res=neg(X)	
Shift	16	10000	Res=SHL Y,X(k-1 to 0)	Shift Left Y of $q \triangleq X(k-1 \dots 0)$ times Res=Y(n-1-q...0)#(q@0) <b>When <math>k = \log_2 n</math></b>
	17	10001	Res=SHR Y,X(k-1 to 0)	Shift Right Y of $q \triangleq X(k-1 \dots 0)$ times Res=(q@0)#Y(n-1...q) <b>When <math>k = \log_2 n</math></b>
Boolean	24	11000	Res=not(Y)	
	25	11001	Res=Y or X	
	26	11010	Res=Y and X	
	27	11011	Res=Y xor X	
	28	11100	Res=Y nor X	
	29	11101	Res=Y nand X	

Table 1: Selected operations

### 3. System Design Micro-Architecture

In this laboratory you will design a module which contains the next three sub-modules:

- Generic Adder/Subtractor module between two vectors Y, X of size n-bit (the default is n=8).
- Generic Shifter module based on Barrel-Shifter n-bit size (the default is n=8).
- Boolean Logic operates bitwise.
- The generic n value can be 4,8,16,32 (set from *tb.vhd* file).
- You are required to design the whole system and make a test bench for testing.


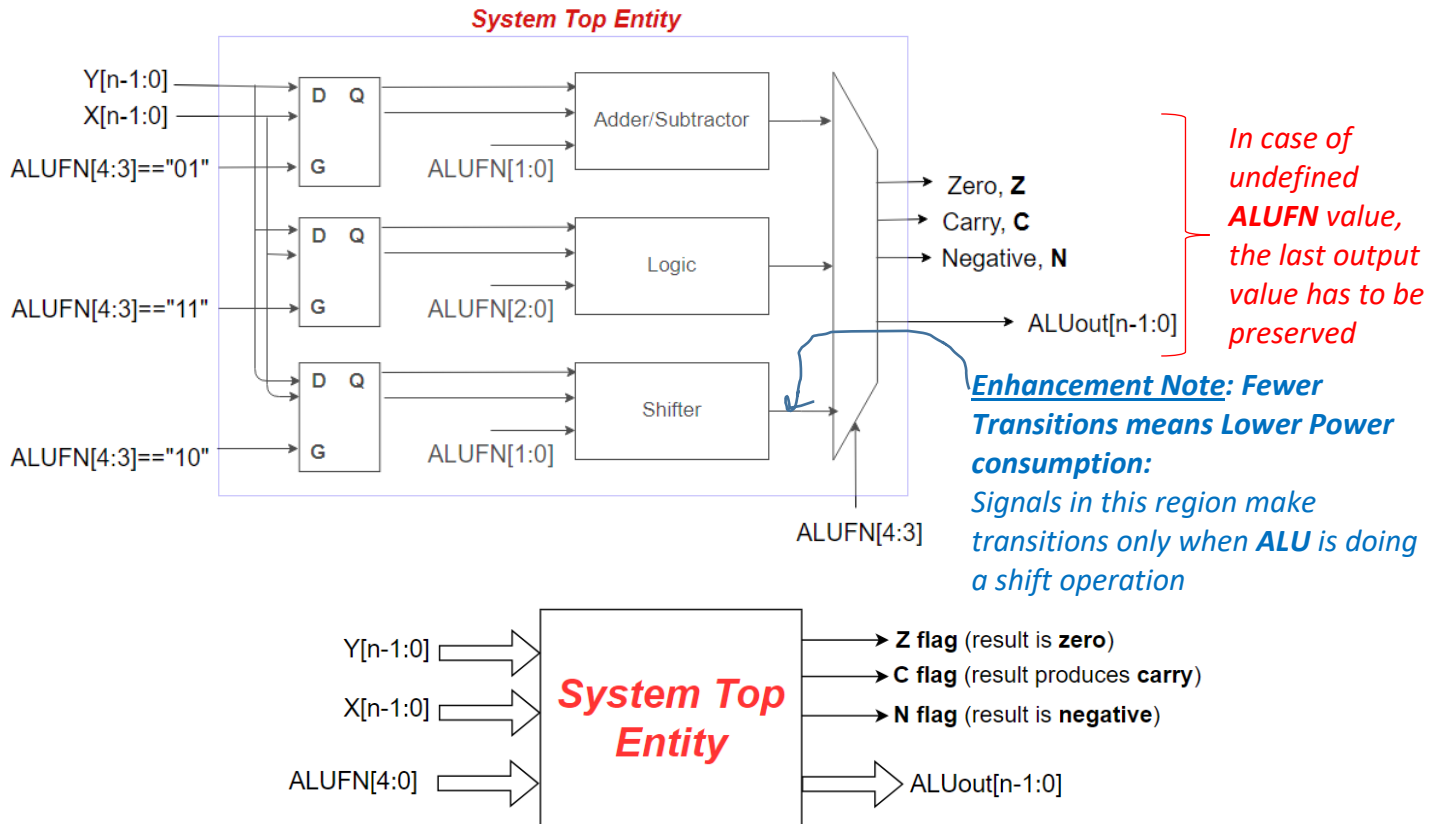


Figure 1 : System top level structure

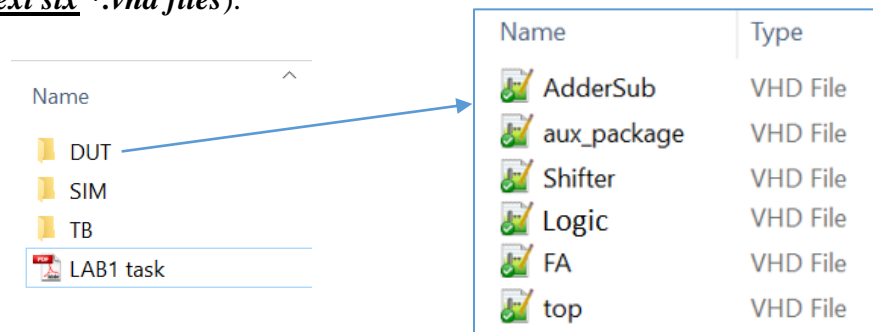
- The Top Level design must be Structural (*your DUT must contain the exact next six \*.vhd files*).



- **Note:** in the given two files **top.vhd**, **aux\_package.vhd** (you can only add code to these files, *you are not allowed to erase anything*).
- The submitted project must be compiled using the given **tb\_ref1.vhd** file (otherwise the submitted project will be considered as a failure).
- The submitted assignments get through copy checking machine, in this case, both sides' assignments will be disqualified.
 
#### 4. Generic Adder/Subtractor module based on a single ripple carry adder:

- You are required to design a Generic Adder/Subtractor between two vectors Y, X of size n-bit (the default is n=8), using the next diagram. The design must be Structural of a least two levels.
- In order to do so, you are asked to use the Generic Adder code that was given in Moodle.



**Note:** this figure illustrates  $Y \pm X$  operation


 


Figure 2: Generic Adder/Subtractor (based on a single ripple carry adder)
 
## 5. Shifter Module based on a single Barrel-Shifter n-bit:

**Note:** using **sll**, **srl** operators are forbidden and causes to disqualification of this clause.

**Hint:** In order to meet the requirements you must use *generate* concurrent statement



**Note:** this figure illustrates the operation *Shift X, Y (2 downto 0)*

 


Figure 3: Example of 8-bit Barrel Shifter

## 6. Test and Timing:


- Design a test bench which tests all the system.
- Analyze the results by zooming on the important transactions in the waveforms. explain these (input/output/internal signals of the system).
- You are welcome to use the Internet also as reference.
- **Good tip for beginners:** Build a test bench for each module you are designing for easy debugging, otherwise you will waste a lot of time for whole system debug.
- The timing of the system will be ideal (means a functional simulation).

## 7. System Output Example (for n=8)


Signal vectors are shown in binary format

ps	delta	/tb/Y	/tb/X	/tb/ALUout	/tb/ALUFN	/tb/Nflag	/tb/Cflag	/tb/Zflag
0	+14	11111111	00000000	01000	11111111	1	0	0
50000	+13	11111110	00000010	01000	00000000	0	1	1
100000	+9	11111101	00000100	01001	11111001	1	1	0
150000	+8	11111100	00000110	01001	11110110	1	1	0
200000	+10	11111011	00001000	01010	11111000	1	0	0
250000	+8	11111010	00001010	01010	11110110	1	0	0
300000	+8	11111001	00001100	10000	10010000	1	1	0
350000	+8	11111000	00001110	10000	00000000	0	0	1
400000	+8	11110111	00010000	10001	11110111	1	0	0
450000	+7	11110110	00010010	10001	00111101	0	1	0
500000	+5	11110101	00010100	11000	00001010	0	0	0
550000	+5	11110100	00010110	11000	00001011	0	0	0
600000	+5	11110011	00011000	11001	11111011	1	0	0
650000	+5	11110010	00011010	11001	11111010	1	0	0
700000	+5	11110001	00011100	11010	00010000	0	0	0
750000	+1	11110000	00011110	11010	00010000	0	0	0
800000	+5	11101111	00100000	11011	11001111	1	0	0
850000	+5	11101110	00100010	11011	11001100	1	0	0
900000	+5	11101101	00100100	11100	00010010	0	0	0
950000	+5	11101100	00100110	11100	00010001	0	0	0
1000000	+5	11101011	00101000	11101	11010111	1	0	0
1050000	+5	11101010	00101010	11101	11010101	1	0	0

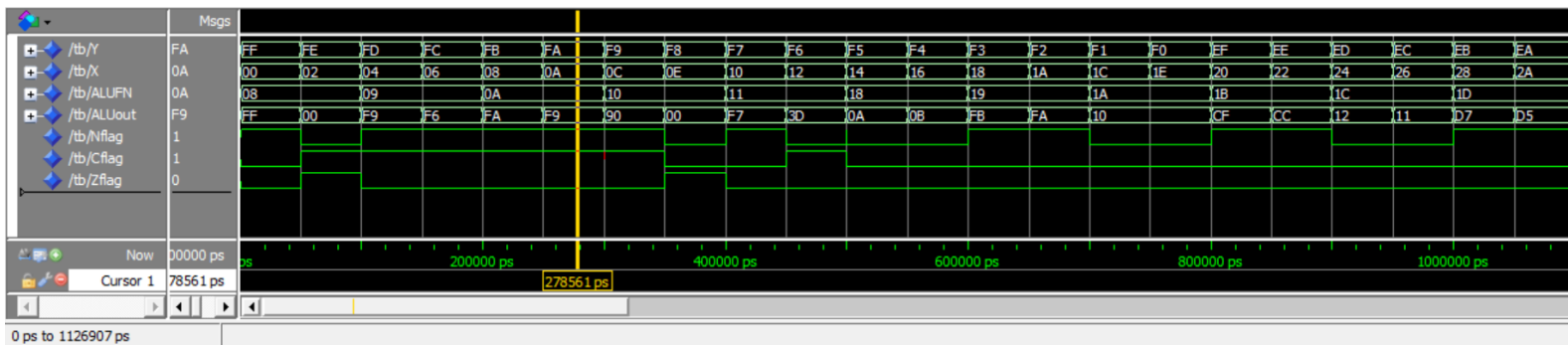
Signals *Y*, *X*, *ALUout* are shown in HEX format (same exact example as above).



 In addition, you are given two test bench files *tb\_ref1.vhd*, *tb\_ref2.vhd* (in TB folder) and their associate do and list files (in SIM folder).




 In order to use golden model based functional verification, you are given [TextDiff](#) application (download and double click the *TextDiff.exe* file) in order to compare your developing design results to the golden model results as part of design developing chain.


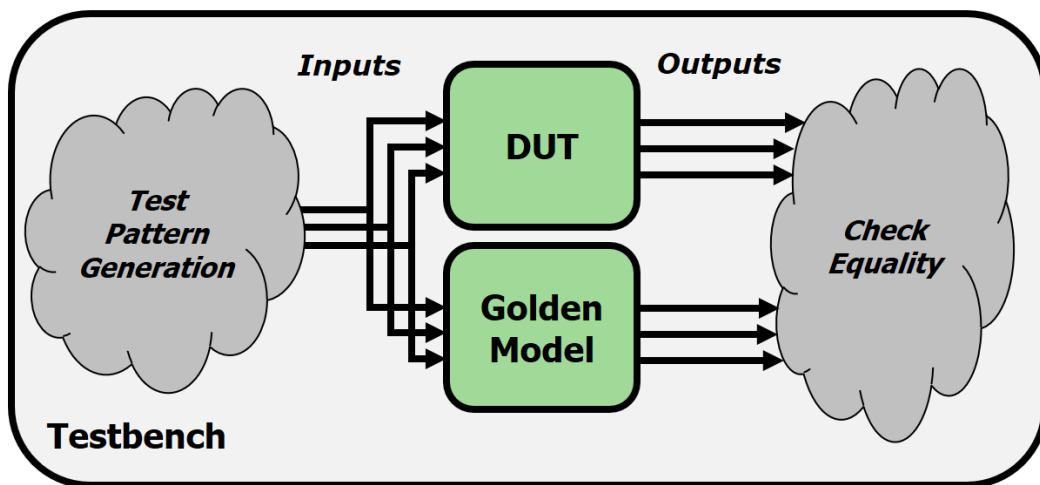
## Automatic Testbench

The DUT **output** is compared against the **golden model**



**Note:** in comparison between the given *tb\_ref1.lst*, *tb\_ref2.lst* files and yours, you should ignore the *delta cycle* column




## 8. Requirements

1. The lab assignment is in pairs (as shown in the inlay file).
2. The design must be well commented.
3. **Important:** For each of two submodules:
  - Graphical description (a square with ports going in and out) and short descriptions.
4. Elaborated analysis and wave forms:
  - Remove irrelevant signals.
  - Zoom on regions of interest.
  - Draw clouds on the waveform with explanations of what is happening (Figure 4).
  - Change the waveform colors in ModelSim for clear documentation  
(Tools->Edit Preferences->Wave Windows).
5. A ZIP file in the form of **id1\_id2.zip** (where id1 and id2 are the identification number of the submitters, and id1 < id2) *must be upload to Moodle only by student with id1* (any of these rules violation disqualify the task submission).
6. The ZIP file will contain (*only the exact next sub folders*):

Directory	Contains	Comments
DUT	Project VHDL files	<b>Only VHDL files of DUT</b> , excluding test bench <b>Note: your project files must be well compiled without errors as a basic condition before submission</b>
TB	<b>Four</b> VHDL files that are used for test bench	AdderSub, Logic, shifter, System (top)
SIM	<b>Four</b> ModelSim DO files (wave, list)	AdderSub, Logic, shifter, System (top)
DOC	Project documentation	<ul style="list-style-type: none"> <li>• <b>readme.txt</b> (list of the DUT *.vhd files with their brief functional description)</li> <li>• <b>pre1.pdf</b> (report file that includes brief explanation of the four modules with their wave diagrams as shown in figure 4)</li> </ul>

Table 2: Directory Structure

 

**Figure 4: Clouds over the waveform**

## 9. Grading Policy

Weight	Task	Description
10%	Documentation	The "clear" way in which you presented the requirements and the analysis and conclusions on the work you've done
90%	Analysis and Test	The correct analysis of the system (under the requirements)

**Table 1 : Grading**

Under the above policies you'll be also evaluated using common sense:

- Your files will be compiled and checked, the system must work.
- Your design and architecture must be intelligent, minimal, effective and well organized.

**For a late submission the penalty is 2<sup>days</sup>**