

CPU Architecture

LAB3 assignment

Digital System Design with VHDL

Hanan Ribo

2/05/2022

Table of contents

1.	Aim of the Task:	3
2.	Assignment definition:	3
3.	Controller based system:	3
4.	File based simulation of DUT:	7
5.	Running Code Example:.....	8
6.	Requirements:	9
7.	Grading Policy	10

1. Aim of the Task:

- System design using concurrent and sequential logic principles using advanced Simulation methods (based on material given in LAB1 and LAB2 tasks).
- Controller design based on methodology of Control and Datapath separation.
- Preparation for LAB4 task – FPGA based design synthesis of the given design.
- Proper analysis and understanding of architecture design.

2. Assignment definition:

In this task, you are required to design a controller-based processing machine in order to run a given program code. The preparation material for this lab has been learned until lecture five and includes in addition to the self-learning material given on a subjects of FSM methodology design and advanced functional verification.

3. Controller based system:

 


Figure 1: Overall DUT structure

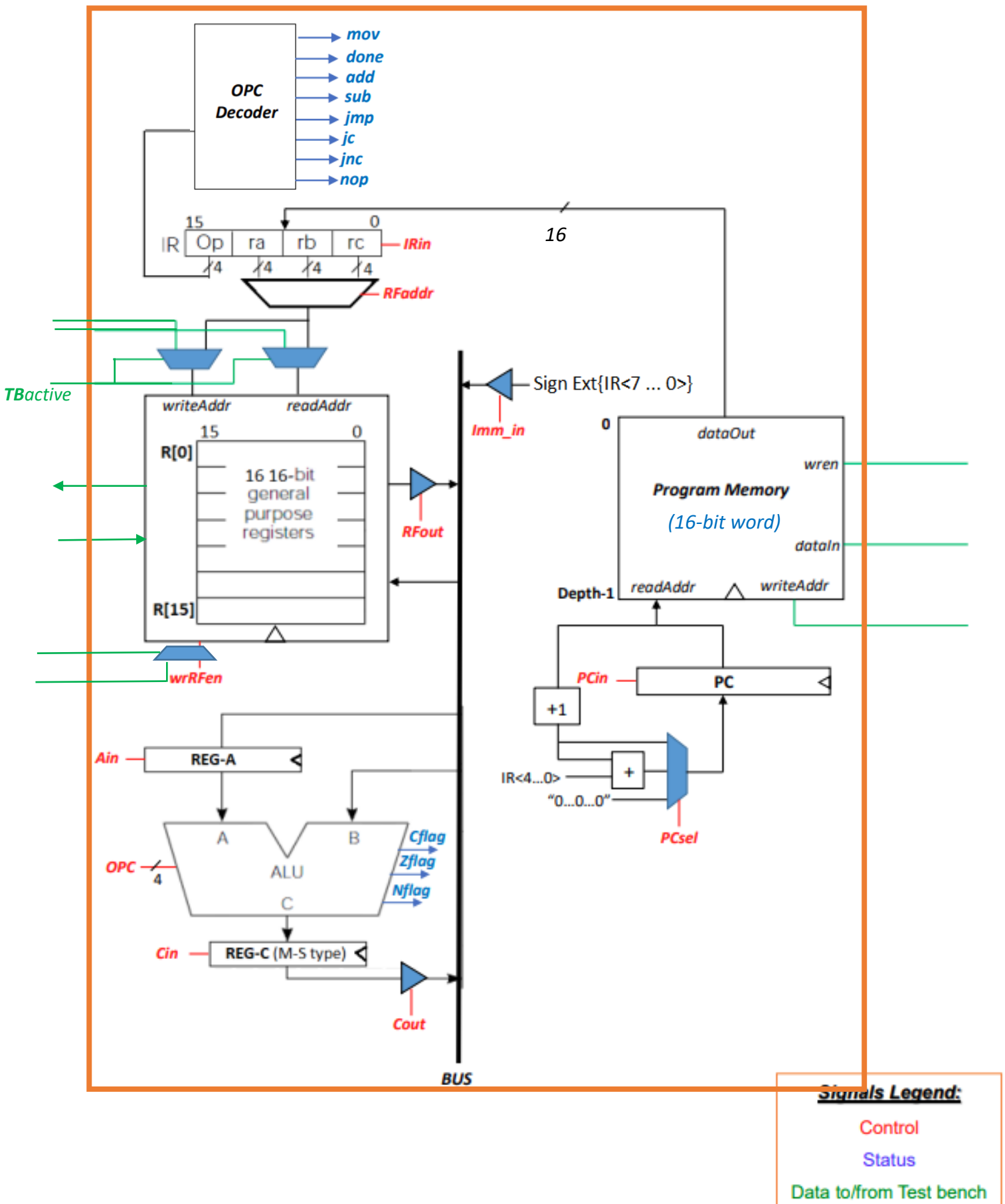


Figure 2: Datapath structure

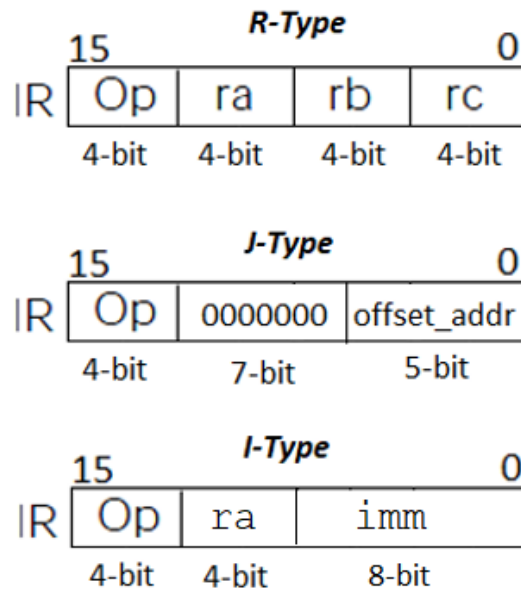


Figure 3: Instruction Formats

Instruction Format	Decimal value	OPC	Instruction	Explanation
R-Type	0	0000	add ra,rb,rc	$R[ra] \leq R[rb] + R[rc]$
	1	0001	sub ra,rb,rc	$R[ra] \leq R[rb] - R[rc]$
	2	0010	nop	$R[0] \leq R[0] + R[0]$
	3	0011	<i>unused</i>	
J-Type	4	0100	jmp offset_addr	$PC \leq PC + 1 + \text{offset_addr}$
	5	0101	jc offset_addr	If(Cflag==1) $PC \leq PC + 1 + \text{offset_addr}$
	6	0110	jnc offset_addr	If(Cflag==0) $PC \leq PC + 1 + \text{offset_addr}$
	7	0111	<i>unused</i>	
I-Type	8	1000	mov ra,imm	$R[ra] \leq \text{imm}$
	9	1001	done	It signals to TB that RF's content is ready to be read

Table 1 : controller ISA

Control Unit

 


Figure 4: Control unit structure


 


Figure 5: Single Port RAM with unregistered output (this structure used for Register File and Program Memory given VHDL code)

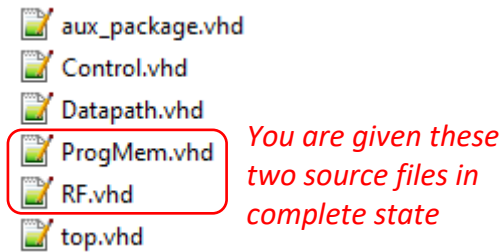
- The given files that you must use in your project:



- ✓ You must use the listed above source files, you are required to fill them up yourself.
- ✓ You can add additional VHDL source code files.
- ✓ Other entities can be designed and modeled behaviorally, structurally, etc.

 4. File based simulation of DUT:

- As depicted in figure 1, in order to simulate the DUT systemly we use file based simulation.
- Two Input and one Output files structure (according the above given figure at clause 3):



5. Running Code Example:

Assembly code

```
1 mov r1,1
2 add r2,r2,r13
3 add r3,r4,r9
4 sub r6,r2,r3
5 jc 2
6 add r6,r1,r0
7 jmp 1
8 add r6,r0,r0
9 done
10 nop
11 jmp -2
```

Equivalent Pseudo code

```
if(R[2]+R[13] >= R[4]+R[9])
    R[6]=0;
else
    R[6]=1;
loop_forever;
```

RAMinit.txt - Notepad

File Edit Format View Help

8101
022D
0349
1623
5002
0610
4001
0600
9000
2000
4FFE

RFininit.txt - Notepad

File Edit Format View Help

0000
0001
0002
0003
0004
0005
0006
0007
0008
0009
000A
000B
000C
000D
000E
000F

RFcontent.txt - Notepad

File Edit Format View Help

0000
0001
000F
000D
0004
0005
0000
0007
0008
0009
000A
000B
000C
000D
000E
000F

Updated values after program run

6. Requirements:

1. The design must be well commented.
2. Elaborated analysis and wave forms:
 - Remove irrelevant signals.
 - Zoom on regions of interest.
 - Draw clouds on the waveform with explanations of what is happening (Figure 4).
 - Change the waveform colors in ModelSim for clear documentation
(Tools->Edit Preferences->Wave Windows).
3. A ZIP file in the form of **id1_id2.zip** (where id1 and id2 are the identification number of the submitters, and id1 < id2) *must be upload to Moodle only by student with id1* (any of these rules violation disqualifies the task submission).
4. The **ZIP** file will contain (*only the exact next sub folders*):

Directory	Contains	Comments
DUT	Project VHDL files	Only VHDL files of DUT , excluding test bench Note: your project files must be well compiled without errors as a basic condition before submission
TB	VHDL files that are used for test bench	One tb.vhd for the Datapath One tb.vhd for the Control unit One tb.vhd for the overall DUT
SIM	ModelSim DO files (wave, list)	One tb.vhd for the Datapath One tb.vhd for the Control unit One tb.vhd for the overall DUT (with Datapath and Control unit signals included)
DOC	Project documentation	<ul style="list-style-type: none">• readme.txt (list of the DUT *.vhd files with their brief functional description)• pre3.pdf (report file that includes brief explanation of the top module with its wave diagrams as shown in figure 4)• designGraph.pdf (elaborated FSM graph of your DUT)

Table 2: Directory Structure

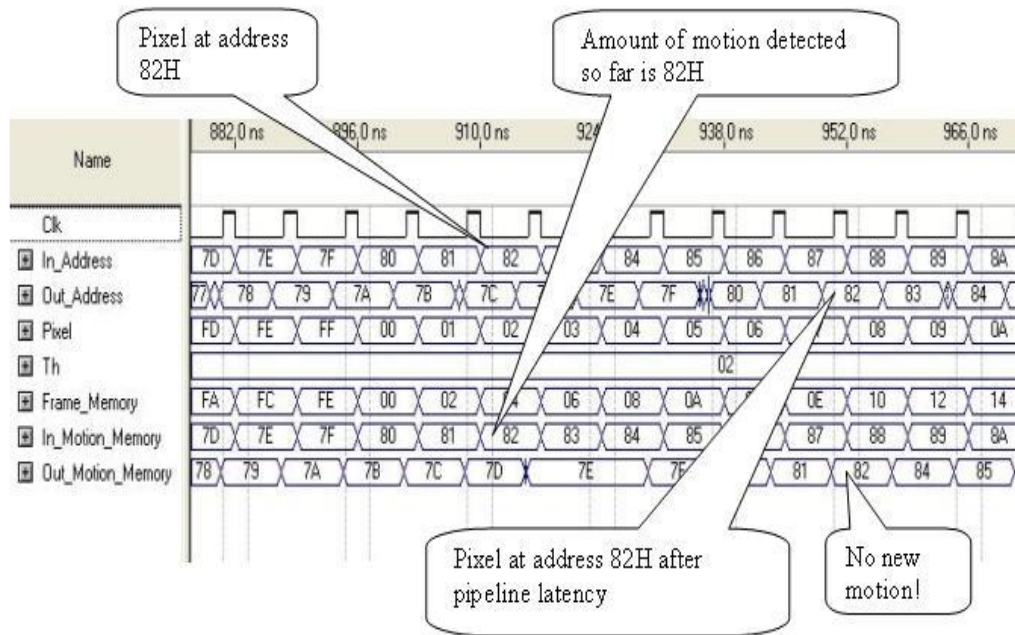


Figure 4: Clouds over the waveform example

7. Grading Policy

Weight	Task	Description
10%	Documentation	The "clear" way in which you presented the requirements and the analysis and conclusions on the work you've done
90%	Analysis and Test	The correct analysis of the system (under the LAB3 SEAT requirements)

Table 3: Grading

Under the above policies you'll be also evaluated using common sense:

- Your files will be compiled and checked, the system must work.
- Your design and architecture must be intelligent, minimal, effective and well organized.